

CS2100

<http://www.comp.nus.edu.sg/~cs2100/>

COMPUTER ORGANISATION

Lecture #17

Combinational Circuits



NUS
National University
of Singapore

School of
Computing

Lecture #17: Combinational Circuits


1. Introduction
2. Analysis Procedure
3. Design Methods
4. Gate-Level (SSI) Design
5. Block-Level Design
6. Summary of Arithmetic Circuits
7. Example: 6-Person Voting System
8. Magnitude Comparator
9. Circuit Delays

1. Introduction

- Two classes of logic circuits
 - Combinational
 - Sequential


- **Combinational Circuit**

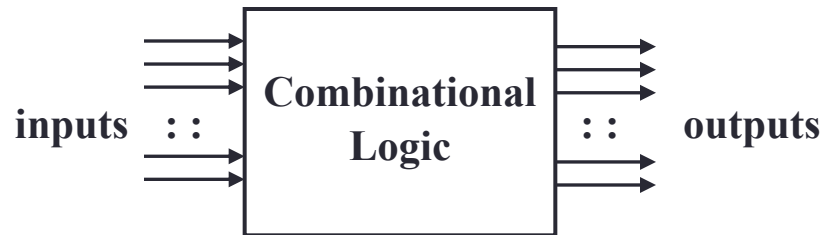- Each output depends entirely on the immediate (present) inputs.



- **Sequential Circuit**

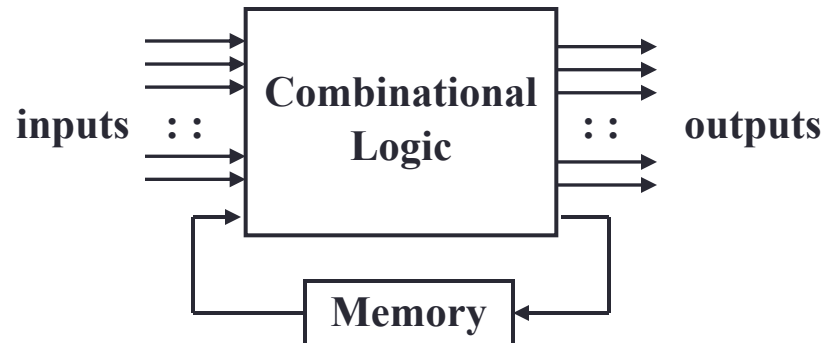
- Each output depends on both present inputs and state.



2. Analysis Procedure

- Given a combinational circuit, how do you analyze its function?

What is this circuit?

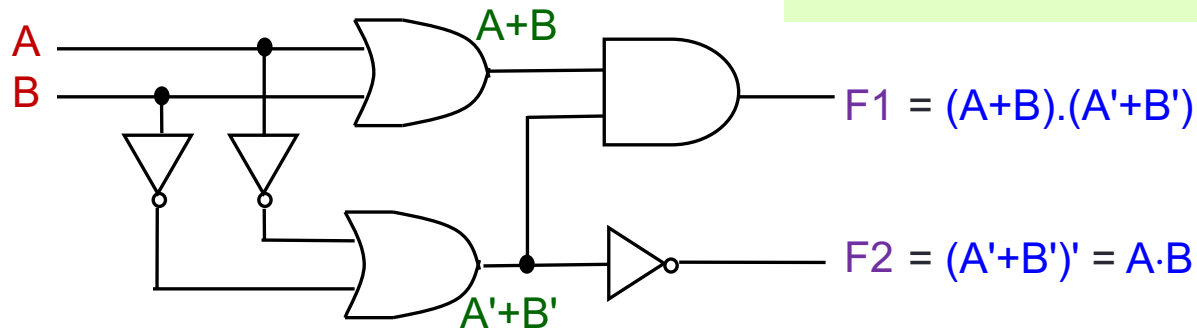

- Steps:
 1. Label the inputs and outputs.
 2. Obtain the functions of intermediate points and the outputs.
 3. Draw the truth table.
 4. Deduce the functionality of the circuit ➡ **Half adder.**

A	B	(A+B)	(A'+B')	F1	F2
0	0	0	1	0	0
0	1	1	1	1	0
1	0	1	1	1	0
1	1	1	0	0	1

3. Design Methods

- Different combinational circuit design methods:
 - Gate-level design method (with logic gates)
 - Block-level design method (with functional blocks)
- Design methods make use of logic gates and useful function blocks
 - These are available as Integrated Circuit (IC) chips.
 - Types of IC chips (based on packing density): SSI, MSI, LSI, VLSI, ULSI.
- Main objectives of circuit design:
 - Reduce cost (number of gates for small circuits; number of IC packages for complex circuits)
 - Increase speed
 - Design simplicity (re-use blocks where possible)

4. Gate-Level (SSI) Design: Half Adder (1/2)


■ Design procedure:

1. State problem

Example: Build a **Half Adder**.

2. Determine and label the inputs and outputs of circuit.

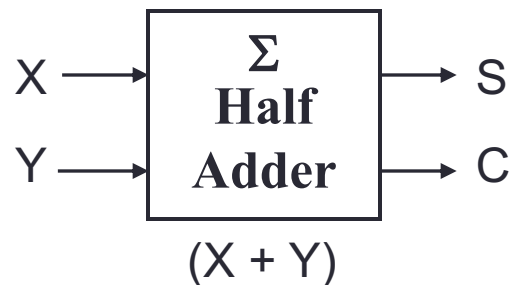Example: Two inputs and two outputs labelled, as shown below.



X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

3. Draw the truth table.

4. Gate-Level (SSI) Design: Half Adder (2/2)

4. Obtain simplified Boolean functions.


Example: $C = X \cdot Y$

$$S = X' \cdot Y + X \cdot Y' = X \oplus Y$$


5. Draw the logic diagram.

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Half Adder

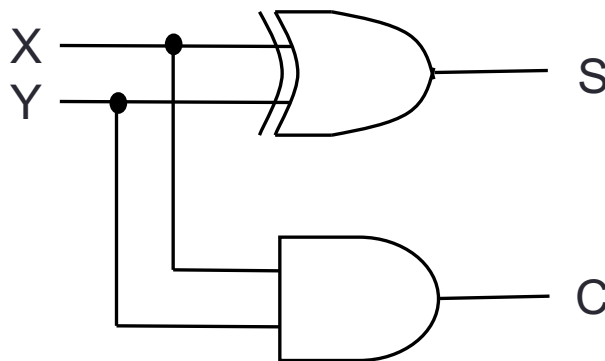

Block diagram
of Half Adder

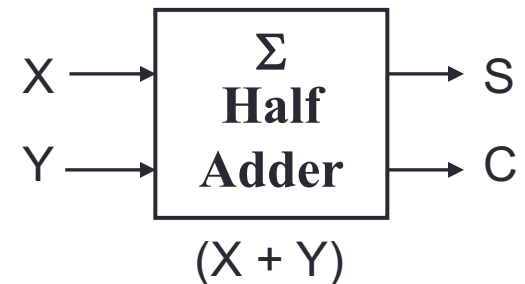


4. Gate-Level (SSI) Design: Full Adder (1/5)

- Half adder adds up only two bits.
- To add two binary numbers, we need to add 3 bits (including the *carry*).

- Example:

		1	1	1		
		0	0	1	1	X
+		0	1	1	1	Y
		1	0	1	0	S

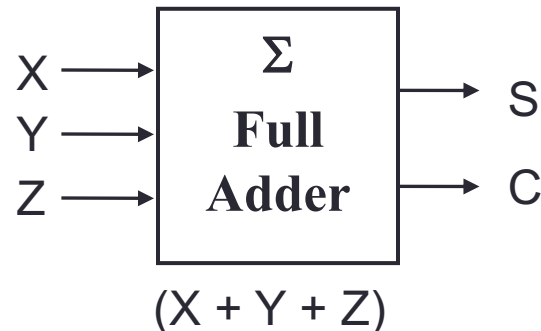- Need **Full Adder** (so called as it can be made from two half adders).



4. Gate-Level (SSI) Design: Full Adder (2/5)

- Truth table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Note:

Z - carry in (to the current position)

C - carry out (to the next position)

C

YZ \ X	00	01	11	10
0	0	0	1	0
1	0	1	1	1

- Using K-map, simplified SOP form:

$$C = X \cdot Y + X \cdot Z + Y \cdot Z$$

$$S = X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y' \cdot Z' + X \cdot Y \cdot Z$$

S

YZ \ X	00	01	11	10
0	0	1	0	1
1	1	0	1	0

4. Gate-Level (SSI) Design: Full Adder (3/5)

- Alternative formulae using algebraic manipulation:

$$\begin{aligned}C &= X \cdot Y + X \cdot Z + Y \cdot Z \\&= X \cdot Y + (X + Y) \cdot Z \\&= X \cdot Y + ((X \oplus Y) + X \cdot Y) \cdot Z \\&= X \cdot Y + (X \oplus Y) \cdot Z + X \cdot Y \cdot Z \\&= \mathbf{X \cdot Y + (X \oplus Y) \cdot Z}\end{aligned}$$


$$\begin{aligned}S &= X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y' \cdot Z' + X \cdot Y \cdot Z \\&= X' \cdot (Y' \cdot Z + Y \cdot Z') + X \cdot (Y' \cdot Z' + Y \cdot Z) \\&= X' \cdot (Y \oplus Z) + X \cdot (Y \oplus Z)' \\&= \mathbf{X \oplus (Y \oplus Z)}\end{aligned}$$

4. Gate-Level (SSI) Design: Full Adder (4/5)

- Circuit for above formulae:

$$C = X \cdot Y + (X \oplus Y) \cdot Z$$
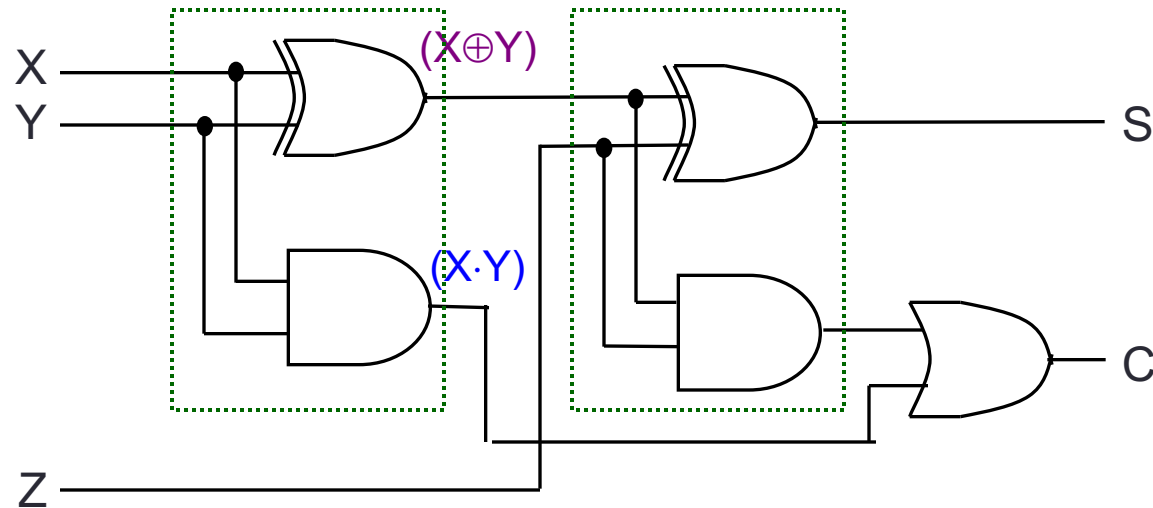
$$S = X \oplus (Y \oplus Z) = (X \oplus Y) \oplus Z \text{ (XOR is associative)}$$




Full Adder made from two Half-Adders (+ an OR gate).

4. Gate-Level (SSI) Design: Full Adder (5/5)

- Circuit for above formulae:

$$C = X \cdot Y + (X \oplus Y) \cdot Z$$

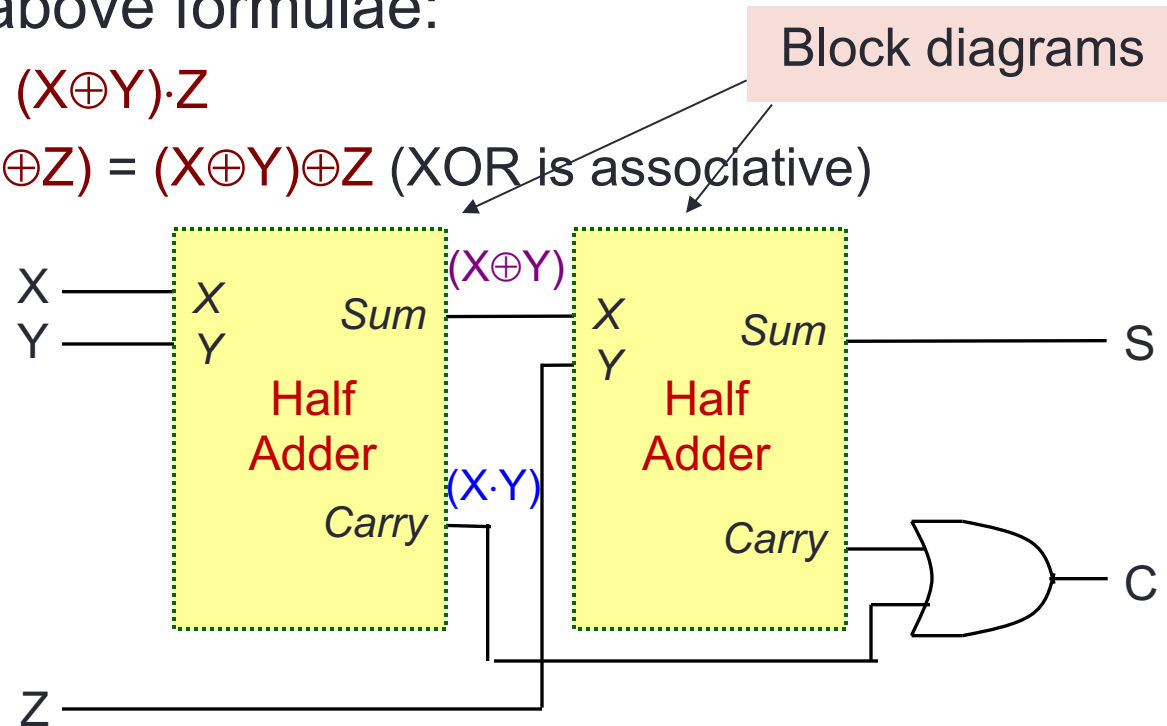
$$S = X \oplus (Y \oplus Z) = (X \oplus Y) \oplus Z \text{ (XOR is associative)}$$



Full Adder made from two Half-Adders (+ an OR gate).

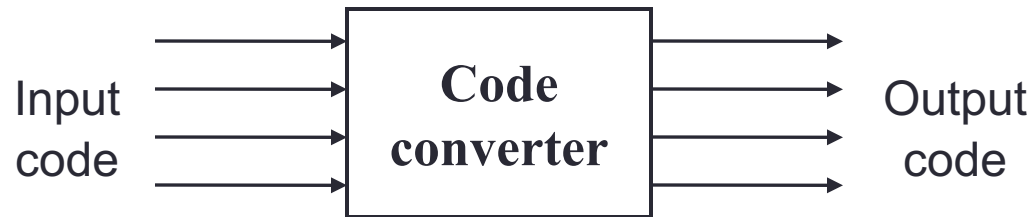4. Gate-Level (SSI) Design: Code Converters

- **Code converter** – takes an input code, translates to its equivalent output code.



- Example: **BCD to Excess-3 code converter**.
 - Input: BCD code
 - Output: Excess-3 code


4. BCD to Excess-3 Code Converter (1/3)

Digit	BCD code	Excess-3 code
0	0000	0011
1	0001	0100
2	0010	0101
3	0011	0110
4	0100	0111
5	0101	1000
6	0110	1001
7	0111	1010
8	1000	1011
9	1001	1100

4. BCD to Excess-3 Code Converter (2/3)


- Truth table:
- K-maps:

	BCD				Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

 


4. BCD to Excess-3 Code Converter (3/3)

W

 

X

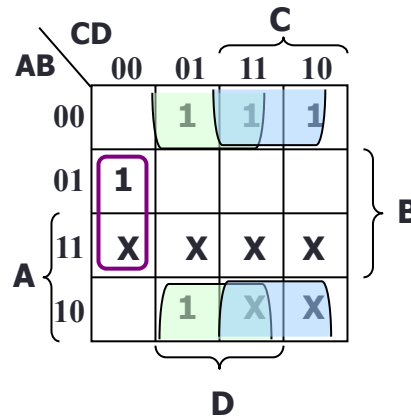


$$W = A + B \cdot C + B \cdot D$$

$$X = B' \cdot C + B' \cdot D + B \cdot C' \cdot D'$$


$$Y = C \cdot D + C' \cdot D'$$

$$Z = D'$$

Y

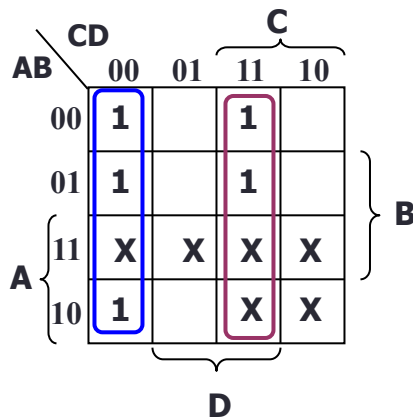

Z

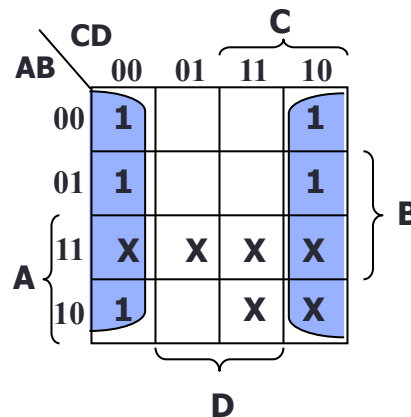


5. Block-Level Design

- More complex circuits can also be built using **block-level** method.
- In general, block-level design method (as opposed to gate-level design) relies on algorithms or formulae of the circuit, which are obtained by decomposing the main problem to sub-problems recursively (until small enough to be directly solved by blocks of circuits).
- First example shows how to create a 4-bit parallel adder using block-level design.
- Using **4-bit parallel adders** as building blocks, we can create the following:
 1. **BCD-to-Excess-3 Code Converter**
 2. **16-bit Parallel Adder**

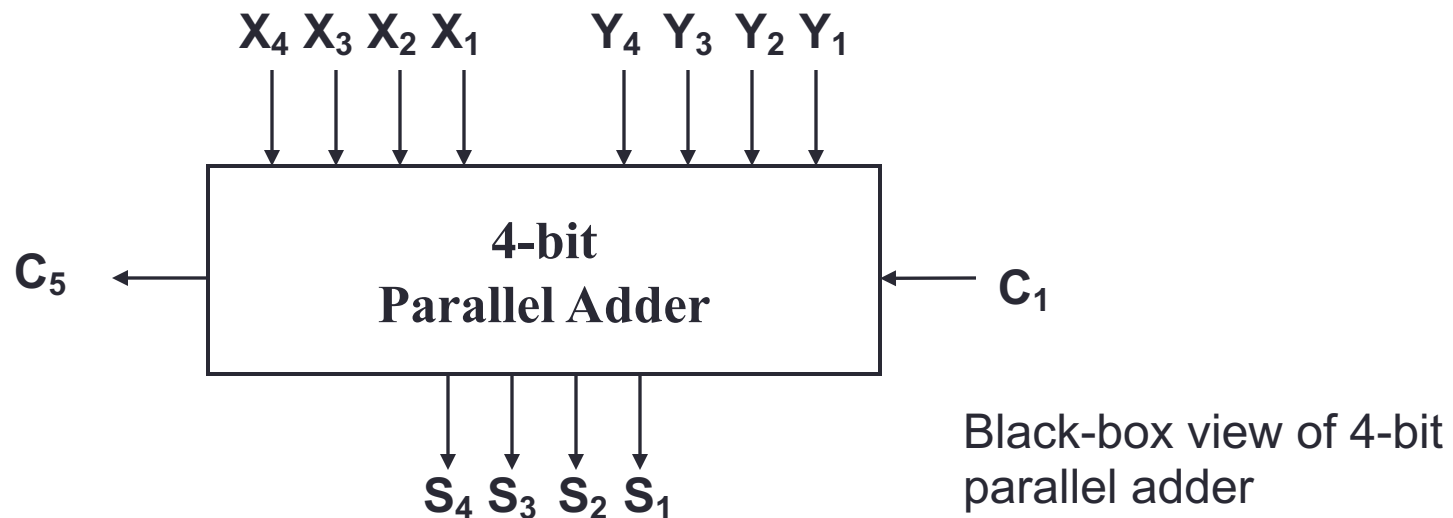5. 4-bit Parallel Adder (1/4)

- Consider a circuit to add two 4-bit numbers together and a carry-in, to produce a 5-bit result.



- 5-bit result is sufficient because the largest result is:
 $1111_2 + 1111_2 + 1_2 = 11111_2$

5. 4-bit Parallel Adder (2/4)

- SSI design (gate-level design) technique should not be used here.
- Truth table for 9 inputs is too big: $2^9 = 512$ rows!

$X_4X_3X_2X_1$	$Y_4Y_3Y_2Y_1$	C_1	C_5	$S_4S_3S_2S_1$
0 0 0 0	0 0 0 0	0	0	0 0 0 0
0 0 0 0	0 0 0 0	1	0	0 0 0 1
0 0 0 0	0 0 0 1	0	0	0 0 0 1
...
0 1 0 1	1 1 0 1	1	1	0 0 1 1
...
1 1 1 1	1 1 1 1	1	1	1 1 1 1

- Simplification becomes too complicated!

5. 4-bit Parallel Adder (3/4)

- Alternative design possible.
- Addition formula for each pair of bits (with carry in),

$$C_{i+1}S_i = X_i + Y_i + C_i$$

has the same function as a full adder:

$$C_{i+1} = X_i \cdot Y_i + (X_i \oplus Y_i) \cdot C_i$$

$$S_i = X_i \oplus Y_i \oplus C_i$$

$$C = \quad \quad \quad 1 \ 1 \ 0 \ 0$$


$$X = \quad \quad \quad 1 \ 0 \ 1 \ 0$$

$$Y = \quad \quad \quad 1 \ 1 \ 1 \ 1$$

$$X + Y = \quad 1 \ 1 \ 0 \ 0 \ 1$$

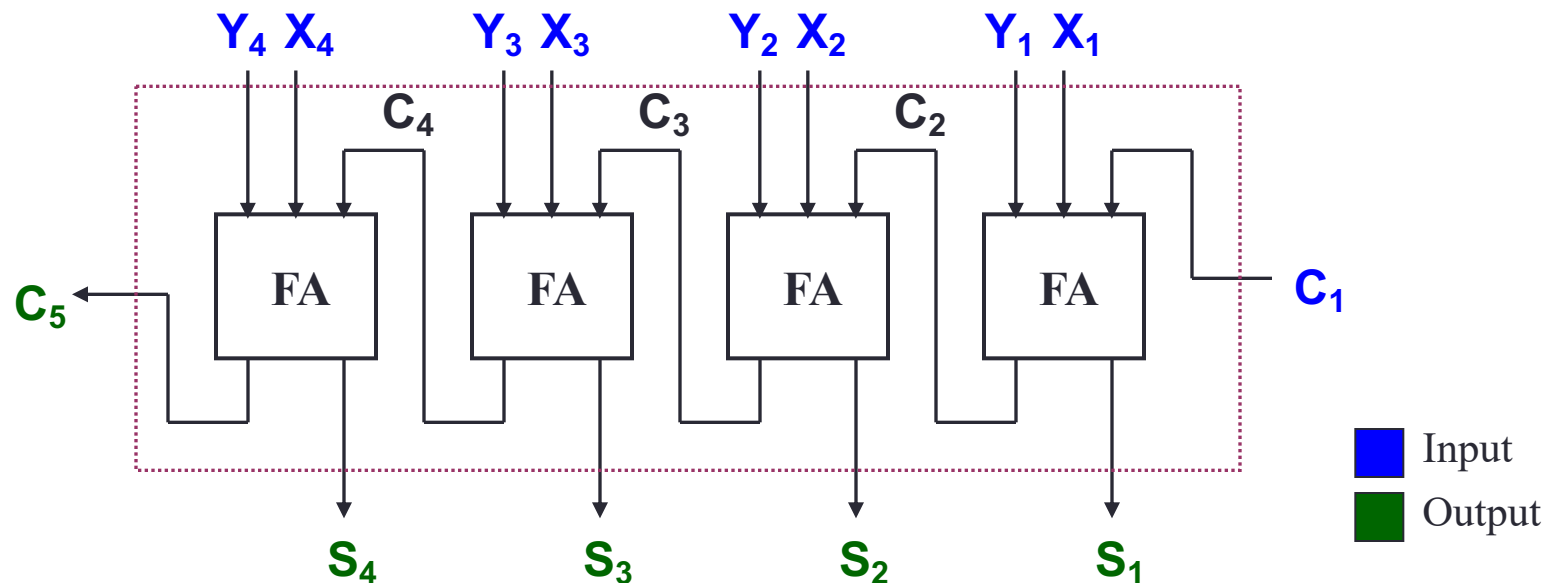5. 4-bit Parallel Adder (4/4)

- Cascading 4 full adders via their carries, we get:



- Note that carry is propagated by cascading the carry from one full adder to the next.
- Called **Parallel Adder** because inputs are presented simultaneously (in parallel). Also called **Ripple-Carry Adder**.

5. BCD to Excess-3 Converter: Revisit (1/2)

- Excess-3 code can be converted from BCD code using truth table:
- Gate-level design can be used since only 4 inputs.
- However, alternative design is possible.
- Use problem-specific formula:


$$\begin{aligned} \text{Excess-3 code} \\ = \text{BCD Code} + 0011_2 \end{aligned}$$

	BCD				Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

5. BCD to Excess-3 Converter: Revisit (2/2)

- Block-level circuit:


A BCD to Excess-3 Code Converter

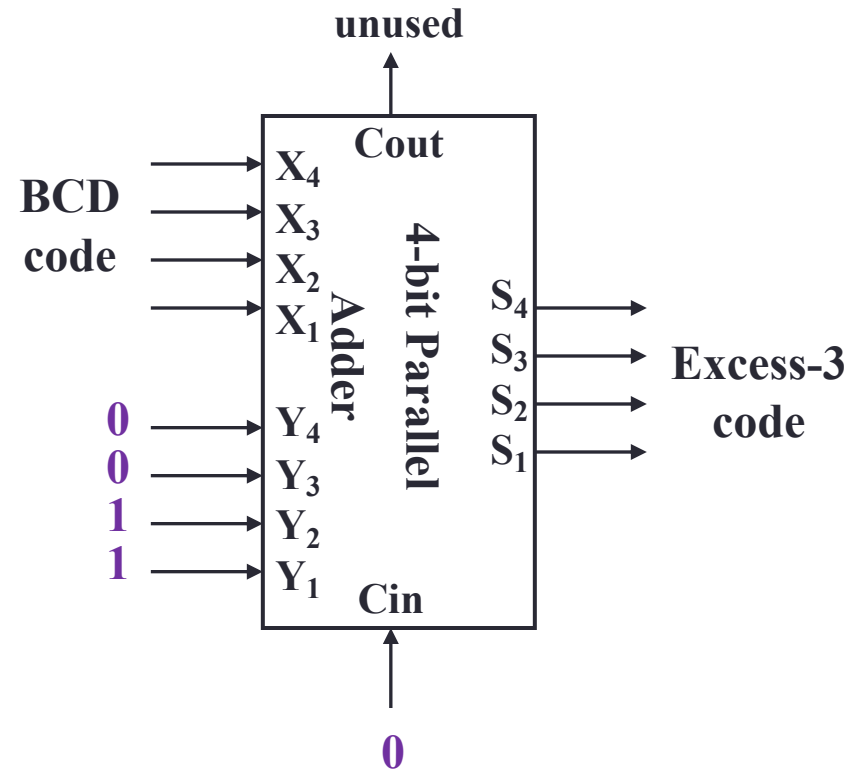


Note: In the lab, input 0 (low) is connected to GND, 1 (high) to Vcc.

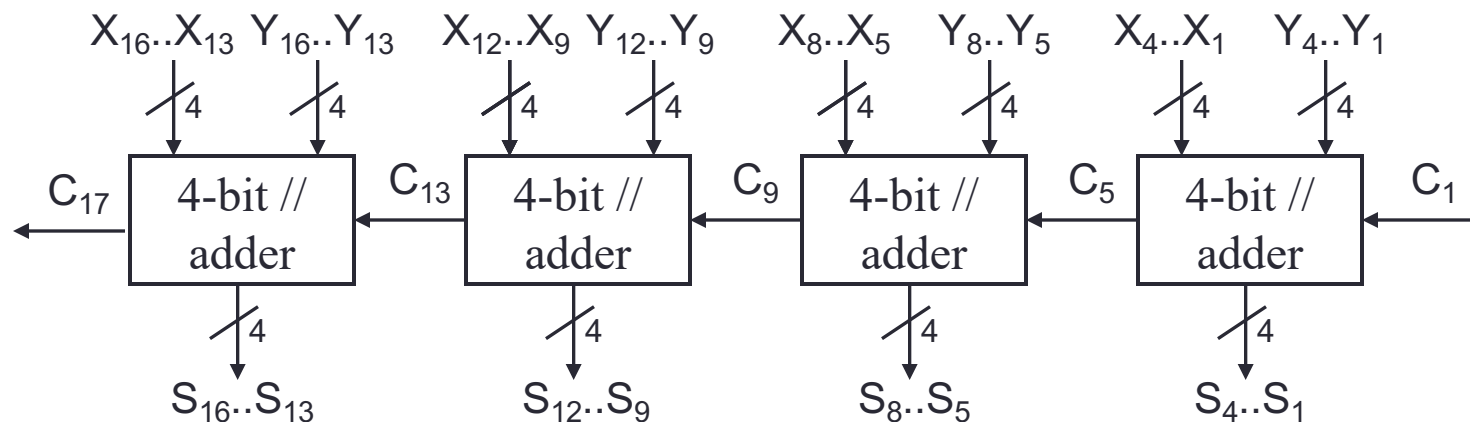5. 16-bit Parallel Adder

- Larger parallel adders can be built from smaller ones.
- Example: A **16-bit parallel adder** can be constructed from four 4-bit parallel adders:








A 16-bit parallel adder

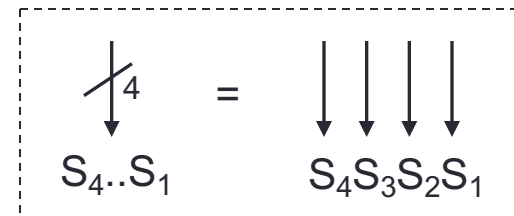

6. Summary of Arithmetic Circuits (1/4)

■ Half adder



x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

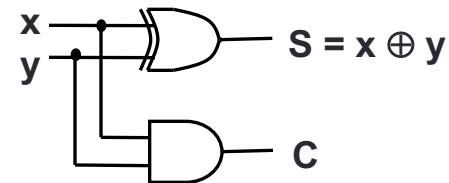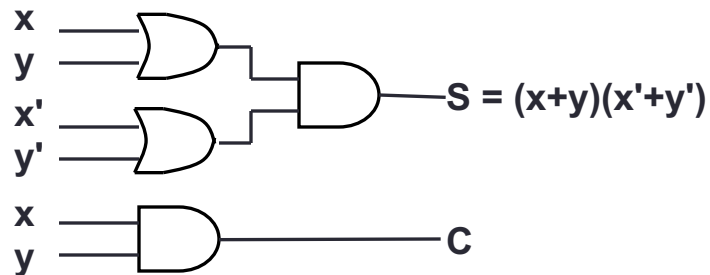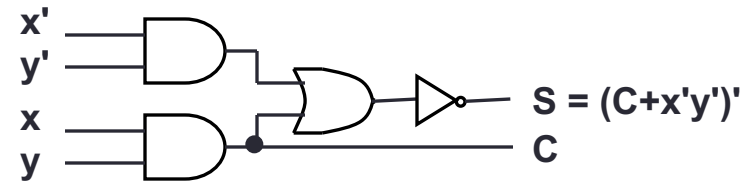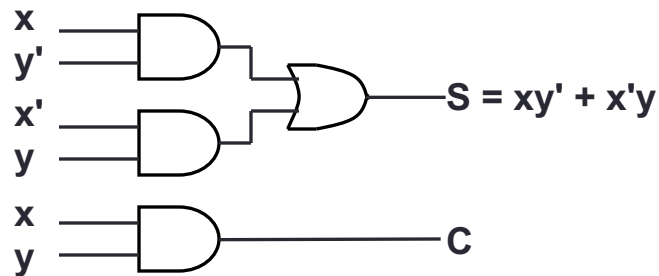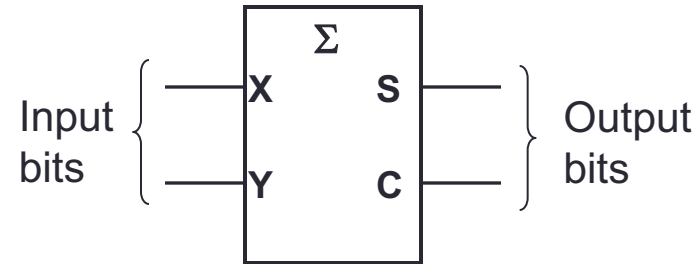

6. Summary of Arithmetic Circuits (2/4)

Full adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

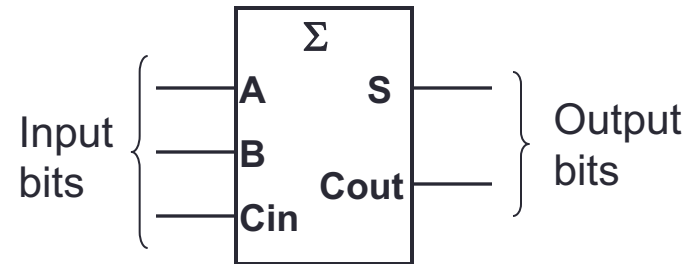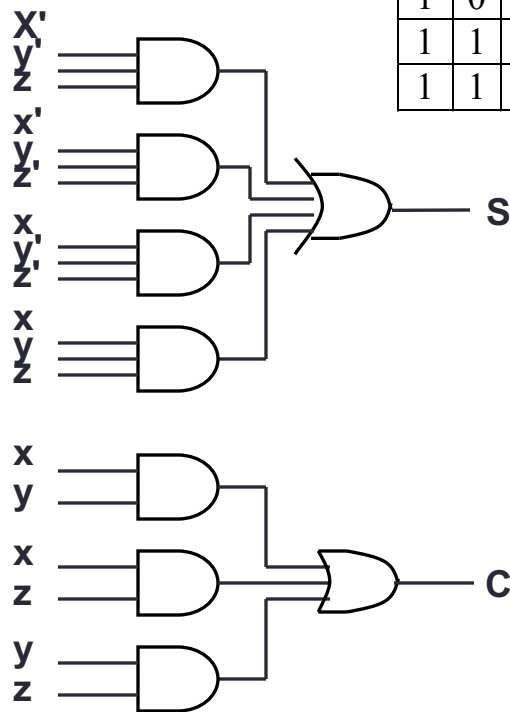


yz	00	01	11	10
x			1	
0			1	
1		1	1	1

$$C = xy + xz + yz$$

yz	00	01	11	10
x				
0		1		1
1	1		1	

$$S = x'y'z + x'yz' + xy'z' + xyz$$

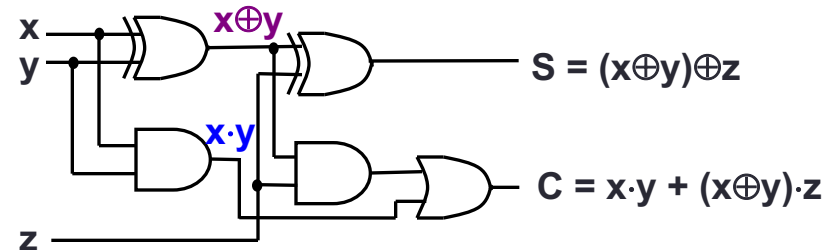



6. Summary of Arithmetic Circuits (3/4)

■ 4-bit parallel adder

Subscript i	4	3	2	1	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}


2 ways:

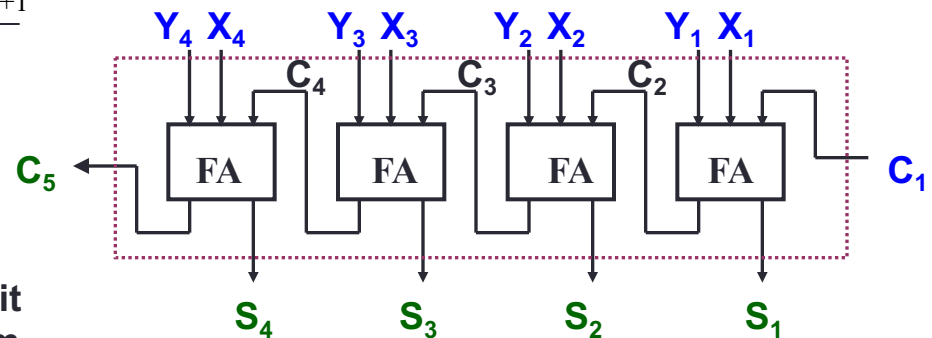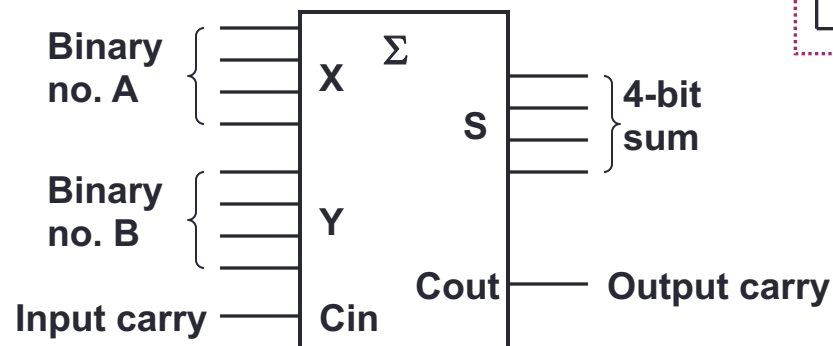- ◆ Serial (one FA)
- ◆ Parallel (n FAs for n bits)



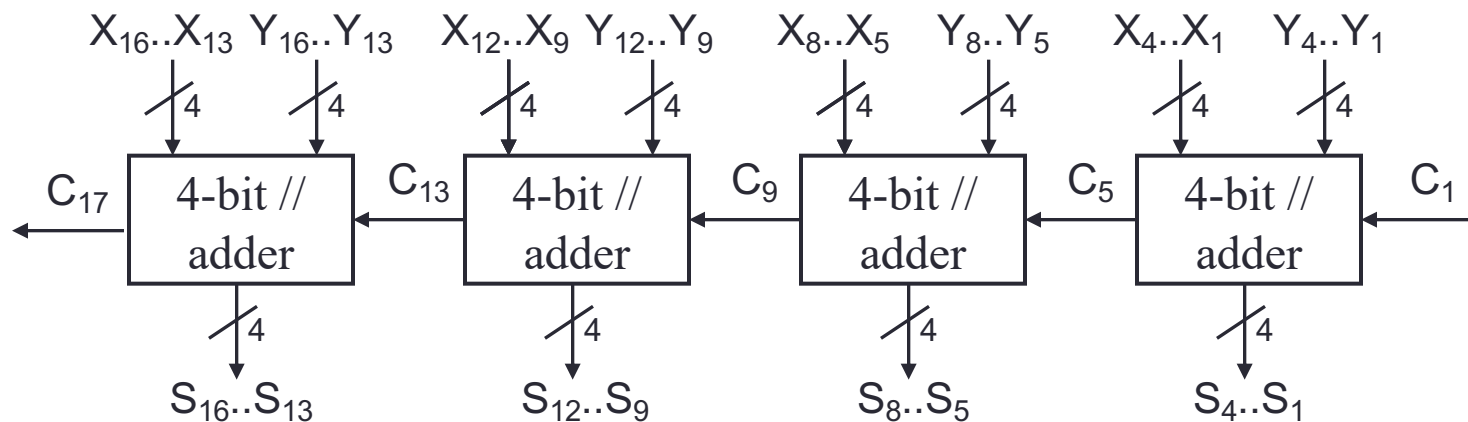
6. Summary of Arithmetic Circuits (4/4)

- Cascading 4 full adders (FAs) gives a 4-bit parallel adder.
 - Classical method: 9 input variables $\rightarrow 2^9 = 512$ rows in truth table!
- Cascading method can be extended to larger adders.
 - Example: **16-bit parallel adder**.



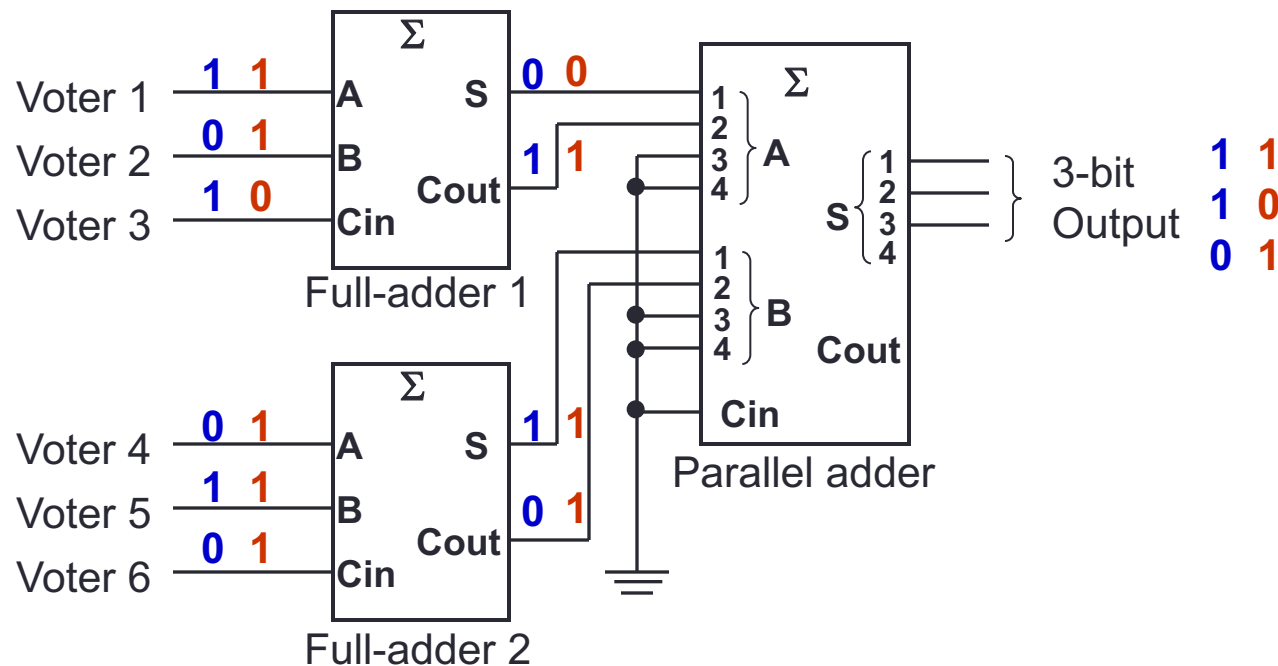7. Example: 6-Person Voting System

- Application: **6-person voting system**.
 - Use FAs and a 4-bit parallel adder.
 - Each FA can sum up to 3 votes.



8. Magnitude Comparator (1/4)

- **Magnitude comparator**: compares 2 unsigned values A and B , to check if $A > B$, $A = B$, or $A < B$.
- To design an n -bit magnitude comparator using classical method, it would require 2^{2n} rows in truth table!
- We shall exploit regularity in our design.
- Question: How do we compare two 4-bit unsigned values $A (a_3a_2a_1a_0)$ and $B (b_3b_2b_1b_0)$?


If $(a_3 > b_3)$ then $A > B$

If $(a_3 < b_3)$ then $A < B$

If $(a_3 = b_3)$ then if $(a_2 > b_2)$...


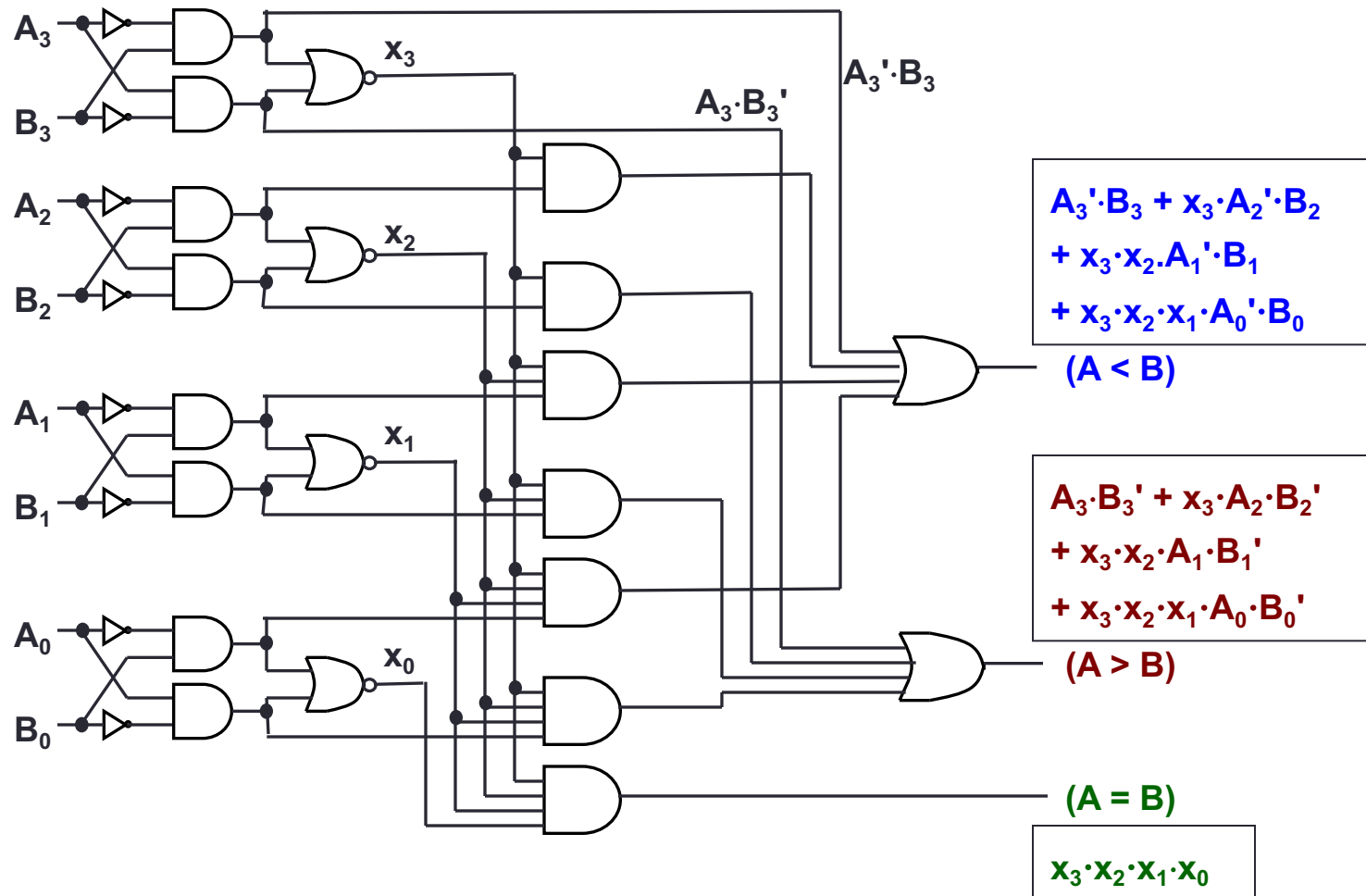
8. Magnitude Comparator (2/4)

Let $A = A_3A_2A_1A_0$, $B = B_3B_2B_1B_0$; $x_i = A_i \cdot B_i + A_i' \cdot B_i'$



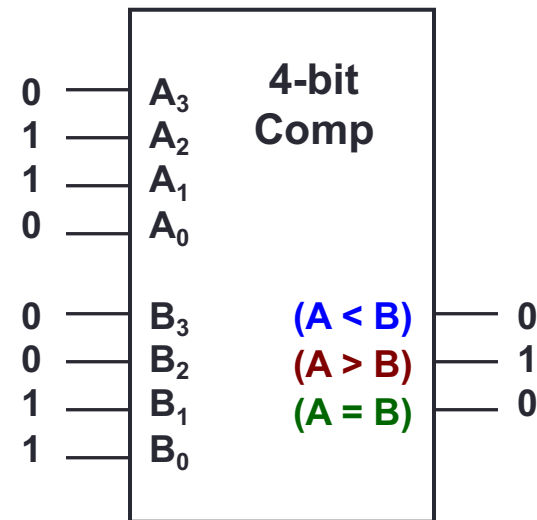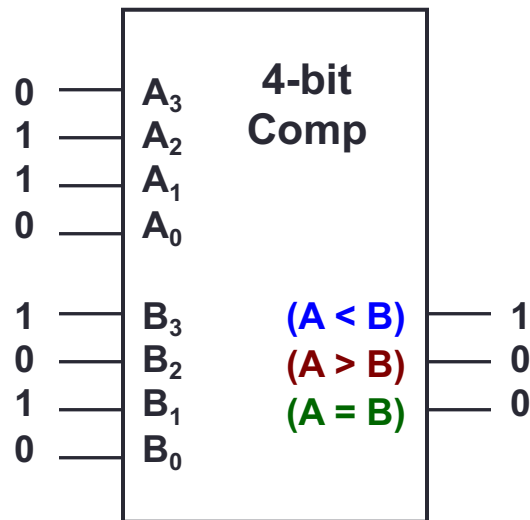
8. Magnitude Comparator (3/4)

- Block diagram of a 4-bit magnitude comparator



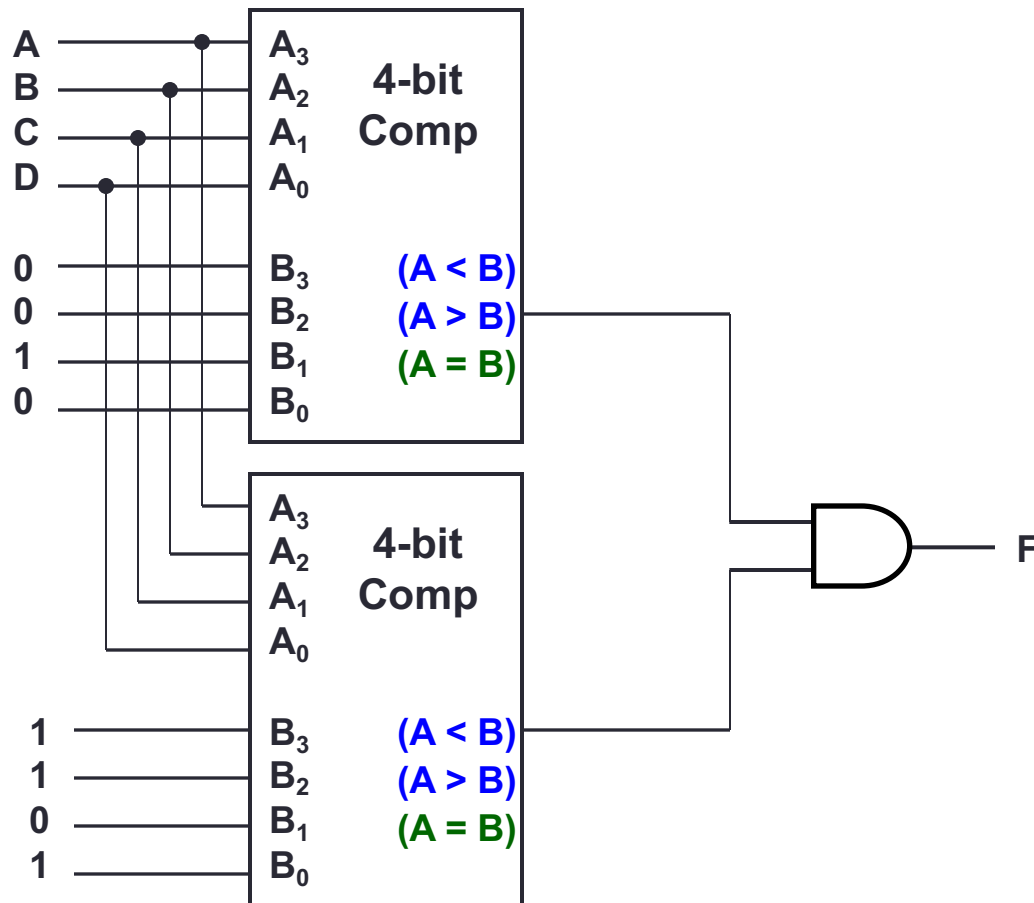8. Magnitude Comparator (4/4)


- A function F accepts a 4-bit binary value $ABCD$, and returns 1 if $3 \leq ABCD \leq 12$, or 0 otherwise. How would you implement F using magnitude comparators and a suitable logic gate?



9. Circuit Delays (1/5)

- Given a logic gate with delay t . If inputs are stable at times t_1, t_2, \dots, t_n , then the earliest time in which the output will be stable is:


$$\max(t_1, t_2, \dots, t_n) + t$$

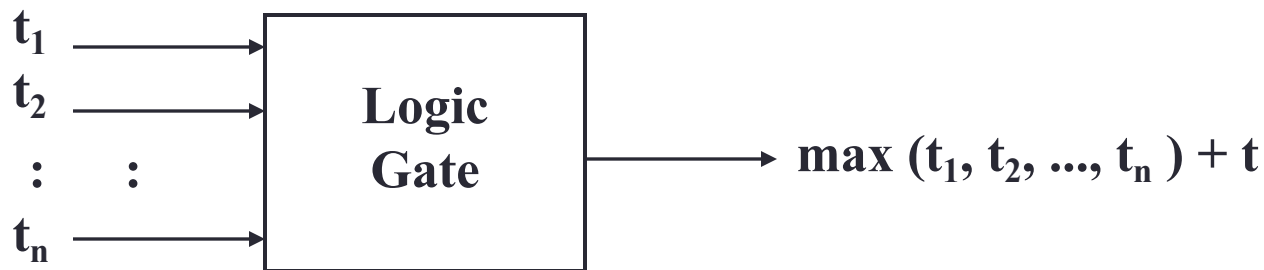

- To calculate the delays of all outputs of a combinational circuit, repeat above rule for all gates.

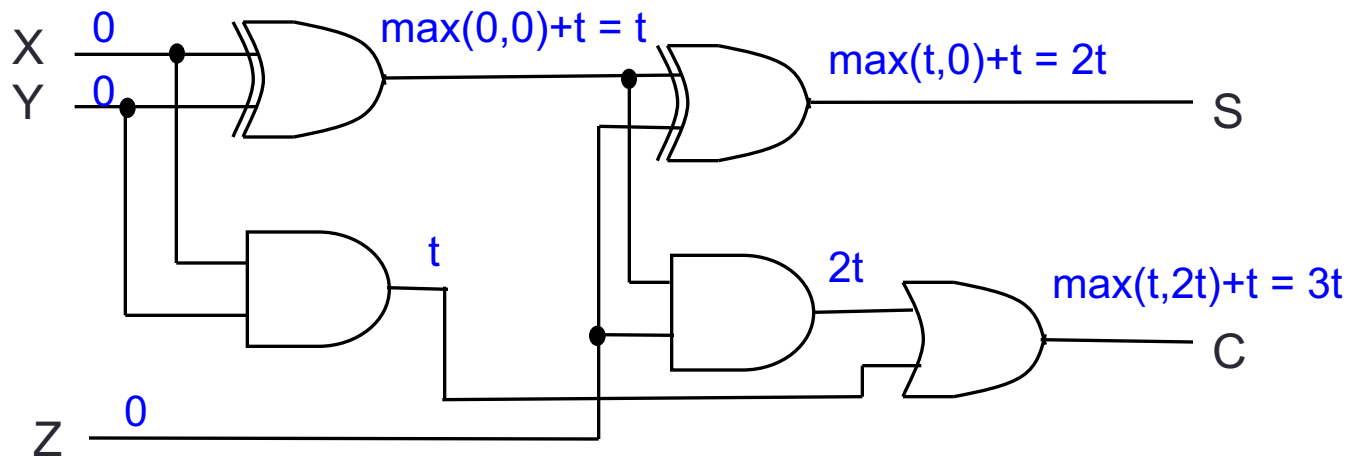9. Circuit Delays (2/5)


- As a simple example, consider the full adder circuit where all inputs are available at time 0. Assume each gate has delay t .



- Outputs **S** and **C** experience delays of **$2t$** and **$3t$** respectively.

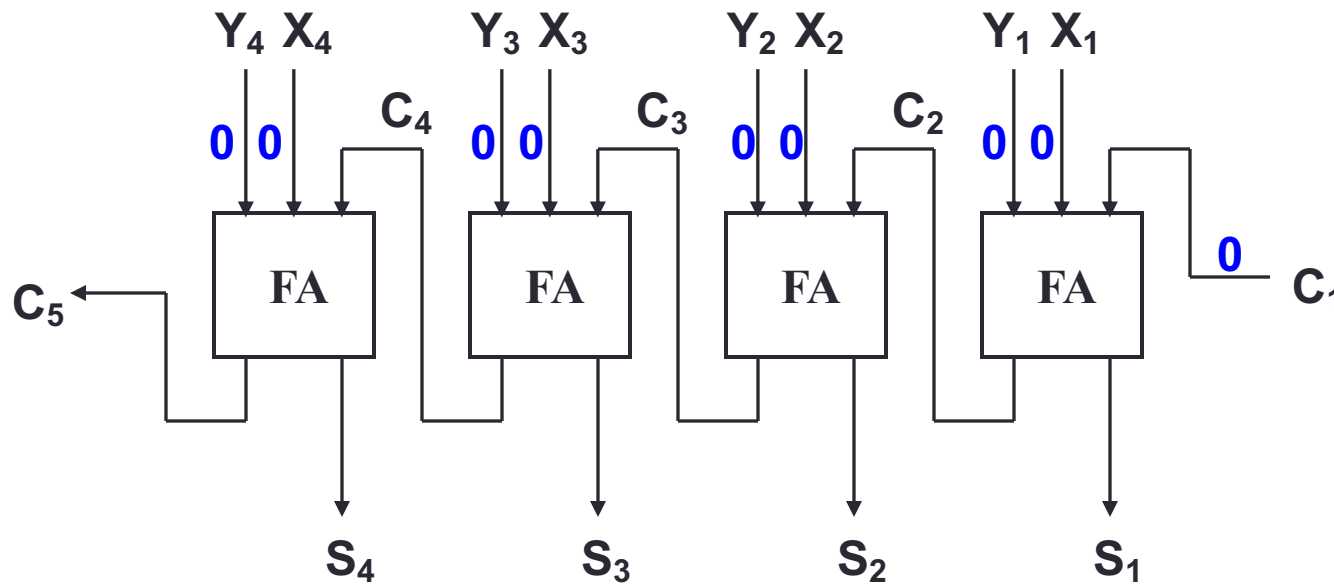9. Circuit Delays (3/5)

- More complex example: 4-bit parallel adder.




9. Circuit Delays (4/5)

- Analyse the delay for the repeated block.




where X_i, Y_i are stable at 0t, while C_i is assumed to be stable at mt.

- Performing the delay calculation:

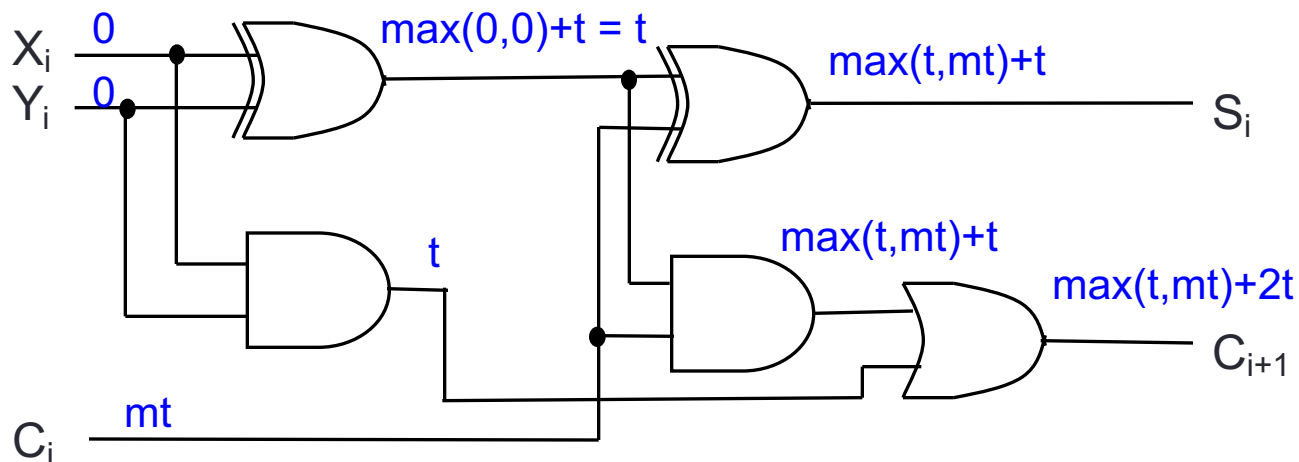

9. Circuit Delays (5/5)

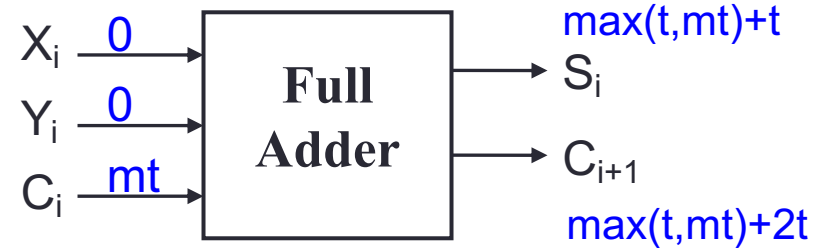

- Calculating:

When $i=1$, $m=0$; $S_1 = 2t$ and $C_2 = 3t$

When $i=2$, $m=3$; $S_2 = 4t$ and $C_3 = 5t$

When $i=3$, $m=5$; $S_3 = 6t$ and $C_4 = 7t$

When $i=4$, $m=7$; $S_4 = 8t$ and $C_5 = 9t$

- In general, an n -bit ripple-carry parallel adder will experience the following delay times:

$$S_n = ((n - 1)2 + 2) t$$

$$C_{n+1} = ((n - 1)2 + 3) t$$

- Propagation delay of ripple-carry parallel adders is proportional to the number of bits it handles.

- Maximum delay: $((n - 1)2 + 3) t$

Quick Review Questions

- DLD pages 128 – 129
Questions 6-1 to 6-4.



End of File